




8/1/24 AGBell





Using NI Elvis and MyDAQ to Support Remote Labs for STEM Education

This presentation will discuss the detailed designs using NI MyDAQs and NI ELVIS IIIs to build circuits that can be remotely accessed from outside of the college. Lab experiments with RC and RL circuits, relays, MyDAQs, and the NI ELVISmx software suite can be used to evaluate RC and RL circuits. Likewise, lab experiments for active filters can be evaluated using NI ELVIS IIIs and NI Measurement Live software. Both the MyDAQ and ELVIS III boxes connect to computers via a USB interface. Each of the four rack-mounted computers is connected to both an ELVIS III and MyDAQ.

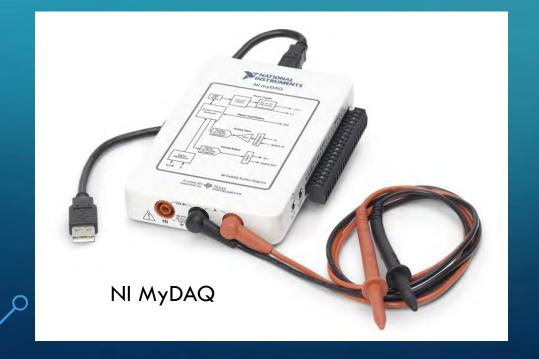




How to use GRE computers and associated equipment using Beyond Trust

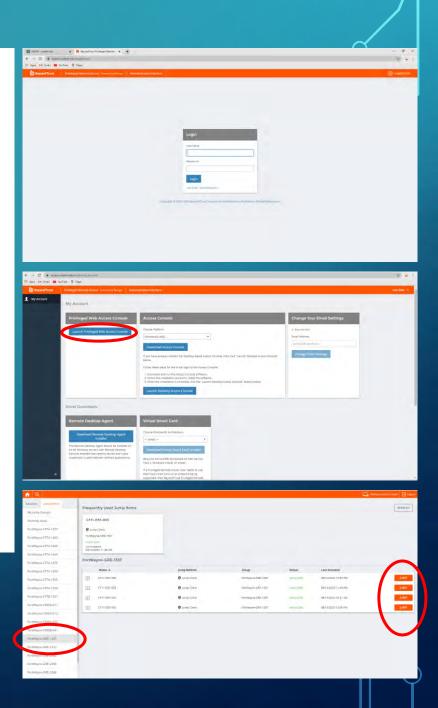- A. To access beyond go to https://access.ivytech.edu/login/login
- B. Select Use SAML Authentication hyperlink under the Login button
- C. Enter your lvy Tech credentials
- D. Select Launch Privileged Web Access Console
- E. Under the Jump Items column highlight FortWayne-GRE-1337 (4 servers should appear numbering 002-005)
- F. Select which server you would like to use. (Depending on slots available) Select the orange JUMP button

We use a common username and password for the 4 GRE computers.


Due the cost of Beyond Trust we will be using a special VPN on the Ivy Tech this fall using Cisco AnyConnect. Students will still a common username and password, but they will need to load the Cisco AnyConnect software on their own computers ...




How to use GRE computers and associated equipment using Beyond Trust (cont)

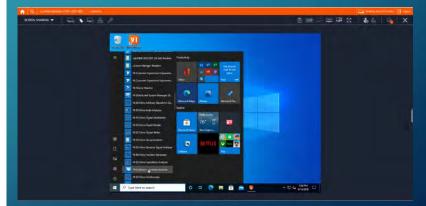- G. The windows login screen should appear.
- H. Treat this window like Windows desktop pick the student account and enter the common password
- II. Setup MyDAQ
- A. National Instruments software suite
- 1. Navigate to windows icon in the left bottom corner
- 2. Find National Instruments drop down menu
- 3. Locate file shortcut NI ELVISmx Instrument Launcher and right click to start
- B. Using the NI ELVISmx Instrument Launcher






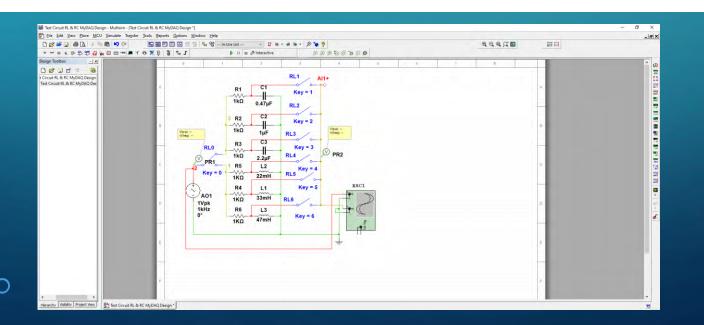- II. Setup MyDAQ (cont)
- B. Using the NI ELVISmx Instrument Launcher
- 1. For an oscilloscope experiment start the following instruments: Oscilloscope >> Function generator >> Digital Writer
- Schematic for the relay logic used for EECT series of experiments. AC input signal is diverted using rly0 to either feed capacitor or inductor side of circuit. The relays 1-6 are used to select the sample being tested.






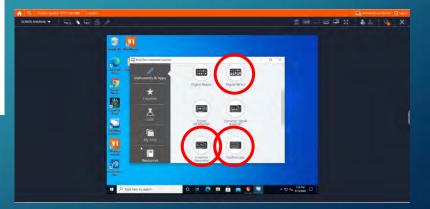

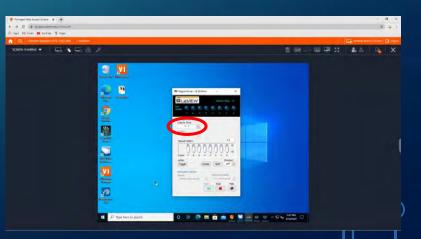- II. Setup MyDAQ (cont)
- B. Using the NI ELVISmx Instrument Launcher
- 3. Function Generator operation type in frequency, Amplitude, then the Run button. (The frequency should appear)
- 4. Oscilloscope first enable channels AlO and Al1 (with nothing selected on digital writer nothing selected both channels should look very similar in frequency and Vpp) Then press the Run button
- 5. Digital Writer open the Lines to Write drop down menu select 0-7







- III. Conduct Experiment
- B. Using the NI ELVISmx Instrument Launcher
- a. Lay out is bit0 switches the function generator between the capacitors and the inductors. Bit1-3 selects capacitors, and bit4-6 selects the inductors to be tested
- b. Each selector bit corresponds to the relay (bit 1 = relay 1, bit 2 = relay 2 ... etc.) After selecting the desired bits press the Run button. You may switch between them
- c. With the selector bit1 activated a 0.47uf and a 1k ohm resistor is being displayed (the signal on Al1(Blue) reflects the change). Take the measurement from channel 1 and compare to the results of the calculations. Note: The nominal value written on component may differ from the actual value.



- III. Conduct Experiment (cont)
- B. Using the NI ELVISmx Instrument Launcher
- d. DON'T FORGET TO DEACTIVATE THE BIT BEFORE MOVING ON TO THE NEXT EXPERIMENT!!!
- e. After Deactivating the bit, move on to the next experiment
- f. To access the inductor side of the experiment first select bit0 (this engages the switching relay), then select an inductor bit4-6
- g. Performing the inductor set of experiments. Bit0 and bit4-6 is actuated, with 1kHz applied at 0.5Vpp.



- III. Conduct Experiment (cont)
- B. Using the NI ELVISmx Instrument Launcher
- 6. AC Frequency Response Bode plots
- a. Within the NI ELVISmx Instrument Launcher window Bode Analyzer and Digital Writer.
- b. Control the relay bits the same way as in previous experiments apply the logic needed to examine the needed components
- c. Set the frequency, turn the cursors on and run this may take a while to finish and the Run button
- d. Set the next experiment logic up and repeat

Stop all running windows and log out

Results need to be saved to your Google Drive!



Key feature

Pros

Very flexibility
Software and hardware are mature.
Cost is low and students can buy their own MyDAQ.
Could support active and passive circuits.
USB interface

Cons

Bandwidth is not real high (20 KHz)
No LCR function
May be a little trick for some students to use.



Ivy Tech designed, and 3D printed a 7-relay holder using Solidworks that supported the used of a full-sized solderless breadboard and seven 5V relays.



